

Washington State University

EE582 Advanced Power Electronics

Project 1

Power Factor Correction Circuits and its Feedback Controller

Name: Chufeng Sun

ID: 11701606

Professor: Dr.Hang Gao

03/25/2022

1. Introduction

With the high modernization, people have a higher requirement for the power quality. Bad power quality would affect electronic devices to not work. Power factor is an important qualification for the power system. Power factor correction is very important because low power factor brings lots of problems to our circuits and power devices. In this project, we will use Matlab/Simulink to design the feedback controllers for single-phase PFC circuit.

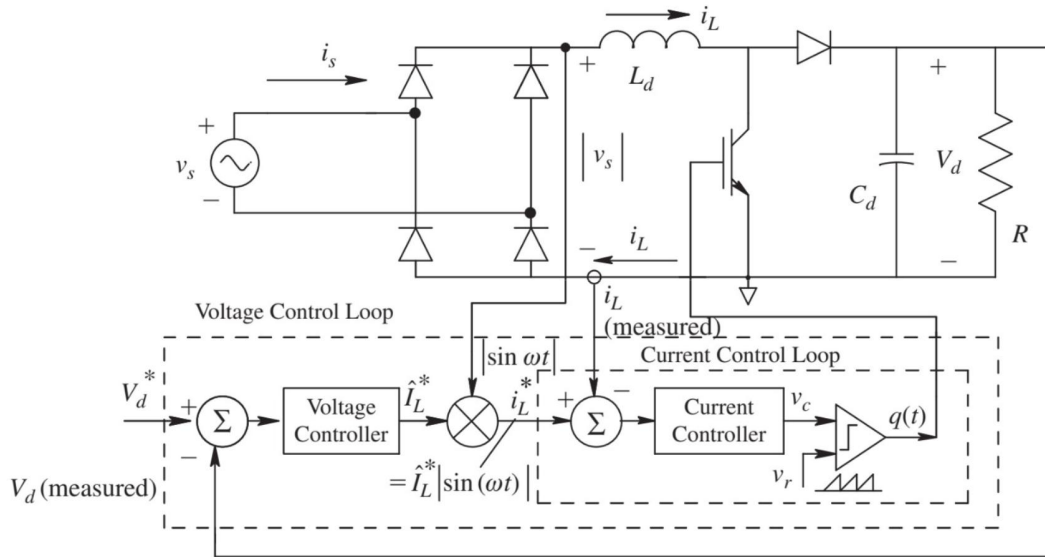


Fig. 1. Single-phase PFC circuit and feedback control.

2. Theory

The basic idea of PFC is using power conversion of high frequency switching mode to make the shape of input current close to sinusoidal wave. In most cases, the correction of power factor is achieved by an independent part which is called PFC (power factor corrector). Typical PFC is to use two cascaded loops: voltage control loop (outer loop) and current control loop (inner loop). The voltage control loop is to regulate the boost DC output voltage and provide the amplitude for the reference to the current controller. This current always remain the residual distortion. The purpose of power factor correction is to make the input current sinusoidal as much as possible to reduce harmonic distortion and its associated losses and bring the power factor in ac circuits close to one.

3. Simulation Results (Matlab/Simulink)

Nominal input ac source voltage - 120 V

Line frequency - 60 Hz

Output voltage - 250 V

Maximum power output - 500 W

Switching frequency - 100kHz
Output filter capacitor - 200 μH
Inductor - 1.5 mH
Full-load equivalent resistance - 125 ohms

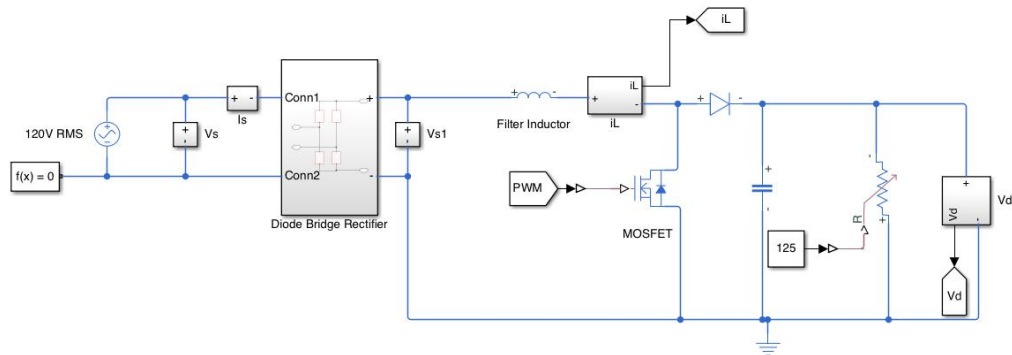


Fig. 2. Simulation of Single-phase PFC circuit.(Matlab/Simulink)

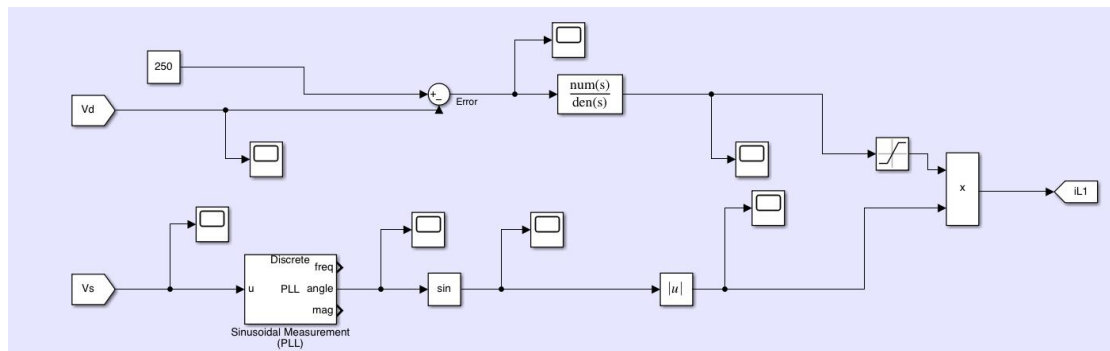


Fig. 3. Voltage Control Loop

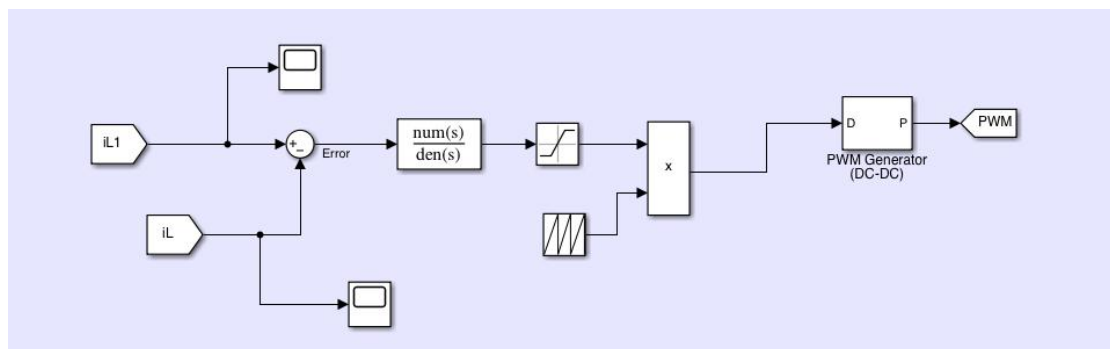


Fig. 4. Current Control Loop

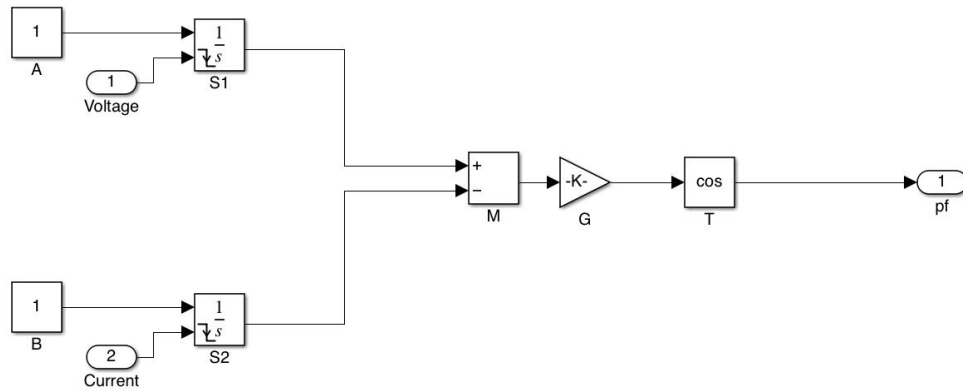


Fig. 5. The Circuit of Calculating Power Factor

Part A)

(1) Design the parameters for the inner current controller given below and show the calculation steps in detail

$$G_i(s) = \frac{k_c (1 + s/w_z)^2}{s (1 + s/w_p)^2}$$

Put the crossover frequency of the inner loop at 10 kHz and the phase margin of 60°.

$$G_{pl}(s) = \frac{V_d}{s \cdot LD} = 0.0000 - 2.6526i$$

$$W_z = 3.6276e + 04$$

$$W_p = 1.0883e + 05$$

$$K_c = 7.8957e + 03$$

$$G_i(s) \approx 7895.7/s$$

(2) Design the parameters for the outer voltage controller given below and show the calculation steps in detail

$$G_v(s) = \frac{k_c (1 + s/w_z)}{s (1 + s/w_p)}$$

Put the crossover frequency of the outer loop at 60 Hz and the phase margin of 60°. Verify if the second-order harmonic (120 Hz) component in the output of the outer voltage controller can be not higher than 5% of the inductor peak current at full load condition.

If yes, keep the parameters for outer voltage controller.

If not, reduce the outer loop crossover frequency, then calculate the parameters again and show the calculation steps.

When $f_c = 60\text{Hz}$;

$$G_{pl}(s) = 0.5 * (V_{in}/V_{out}) * (R/2)/(1 + (s/1/(R * C/2))) = 0.9141 - 4.3076i$$

$$W_z = 144.6409$$

$$W_p = 982.5871$$

$$K_c = 32.8466$$

Assume $G' = 0.05 \times 4 \times 2 \times \pi \times 120 \times C \times V_0 / V_{in} = 0.0444$;

$$G_v = G_p / (2 \times \pi \times 120 \times j) = 0.1834$$

$G_v > G'$. So that, we need to change the crossover frequency. By calculate we find as

$$f_c = 27 \quad G_v < G'.$$

$$G_v = 0.0440$$

And

$$G_v(s) \approx (9.3282 + 0.107s)/s$$

Part B)

Develop a simulation program for the single-phase PFC. Run your simulation program for tasks given in Table 1.

1) For each of the tasks, plot waveforms (2 cycles each) for the utility voltage V_s (V) and line current I_s (A) and calculate the input power factor; plot the waveform for the dc voltage V_d (V). 2) Plot the harmonic spectrum (0 to

1. Task 1

Full Load - 125 ohms

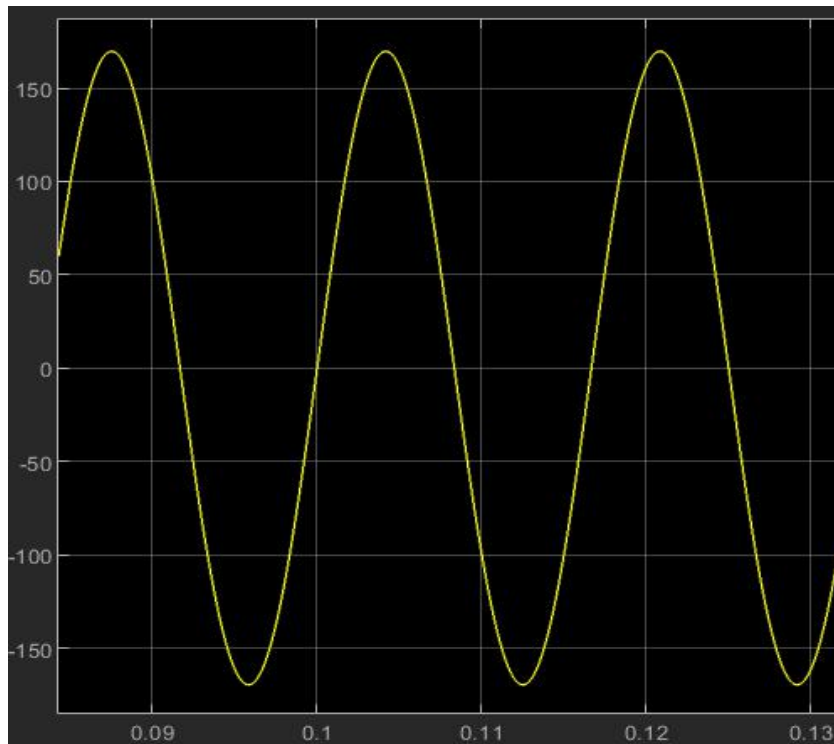


Fig. 5. Vs for Full load

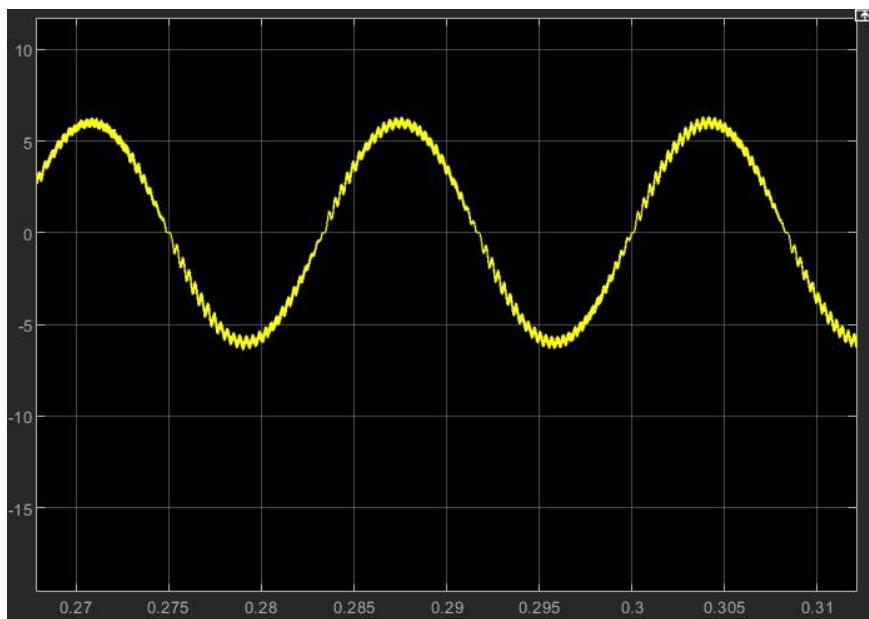


Fig. 6. Is for Full load

Power Factor=1

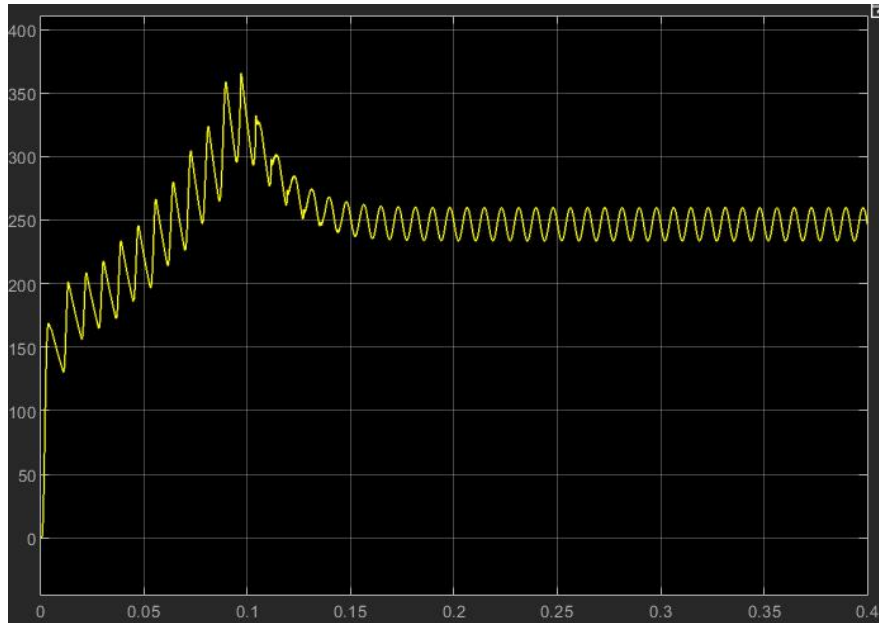


Fig. 7. V_d for Full Load

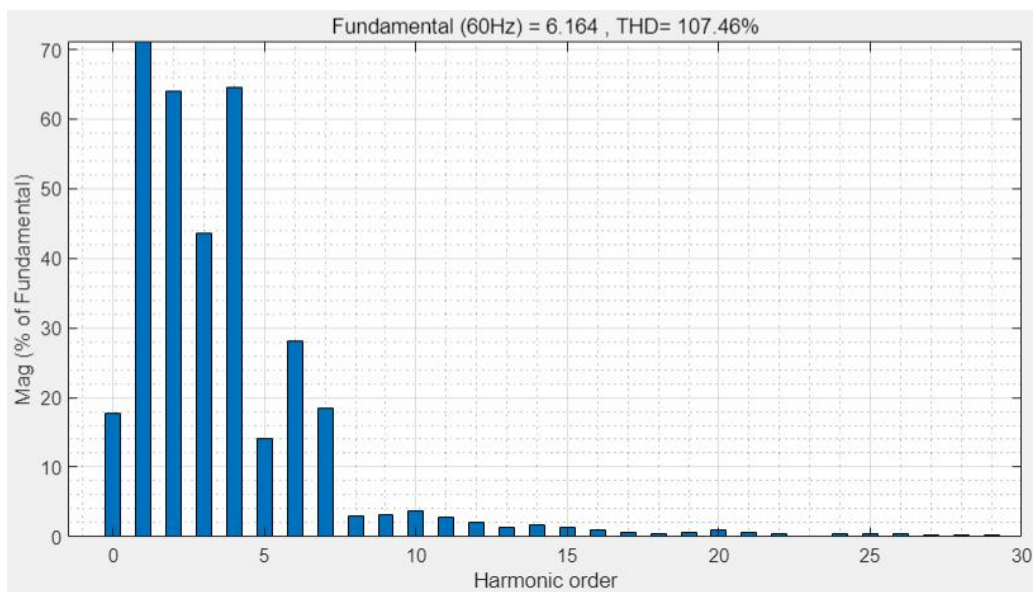


Fig. 8. The harmonic spectrum of I_s
THD of I_s =107.46%

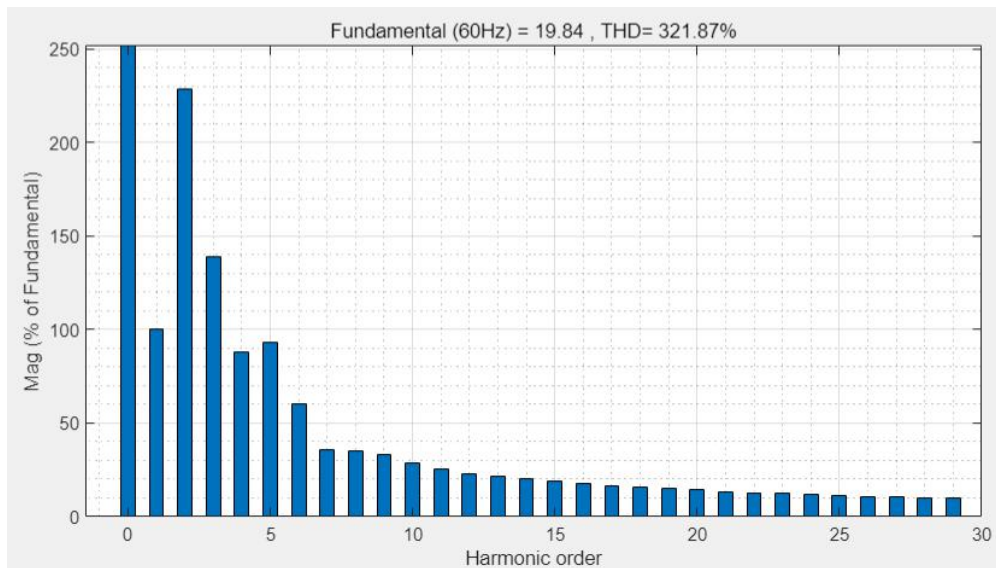


Fig. 9. The harmonic spectrum of Vd

2.Task 2

Half Load - 250 ohms

$$G_v(s) \approx (6.1054 + 0.0955s)/s$$

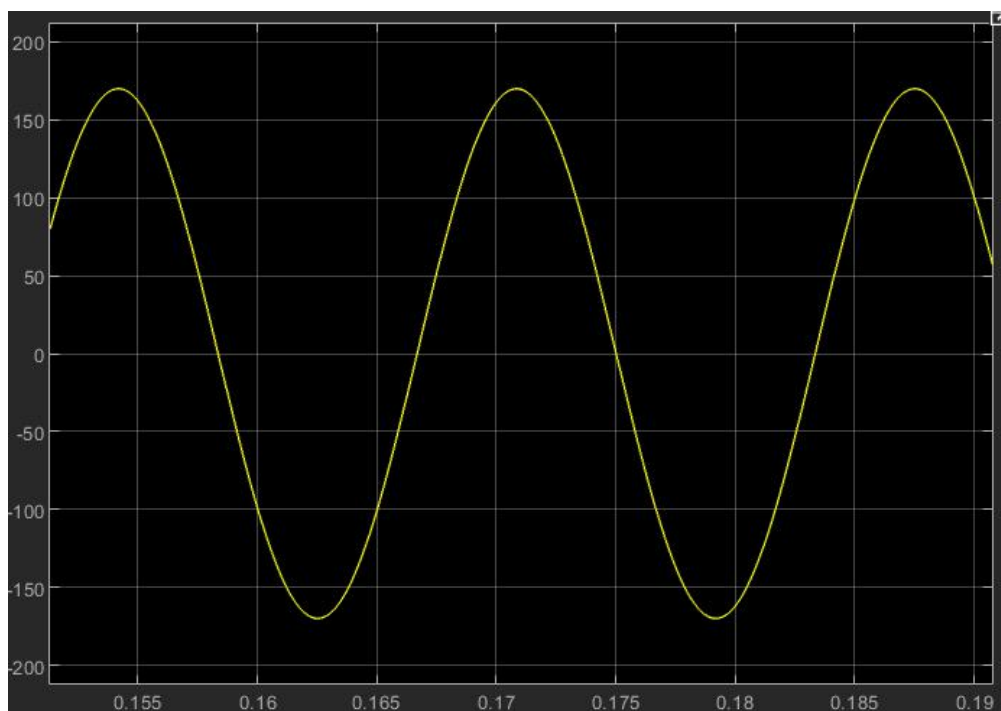


Fig. 10. Vs for Half load

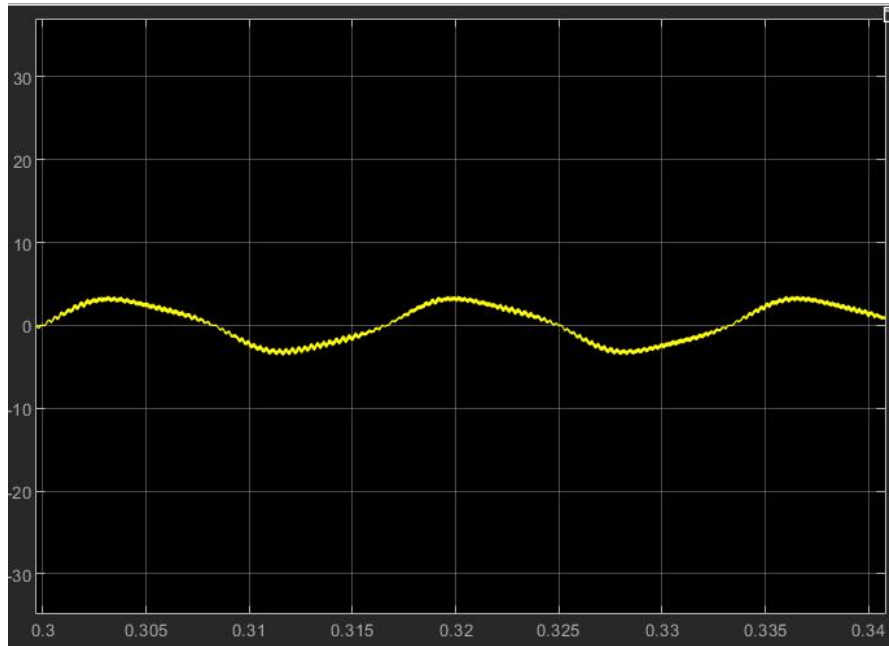


Fig. 11. I_s for Half load
Power Factor=1

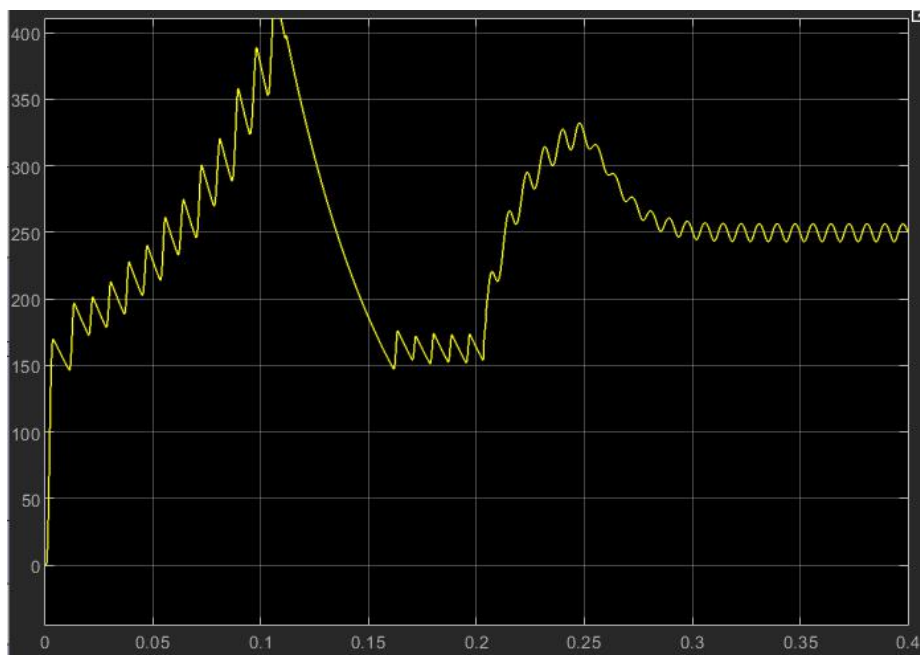


Fig. 12. V_d for Half load

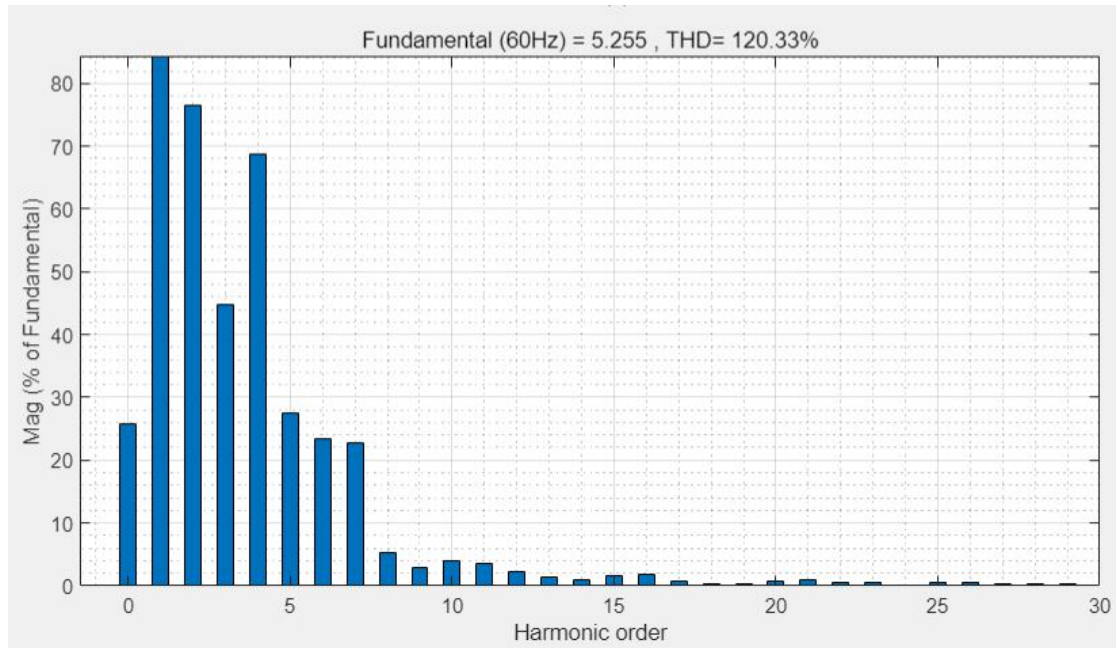


Fig. 13. The harmonic spectrum of Is
THD of Is = 120.33%

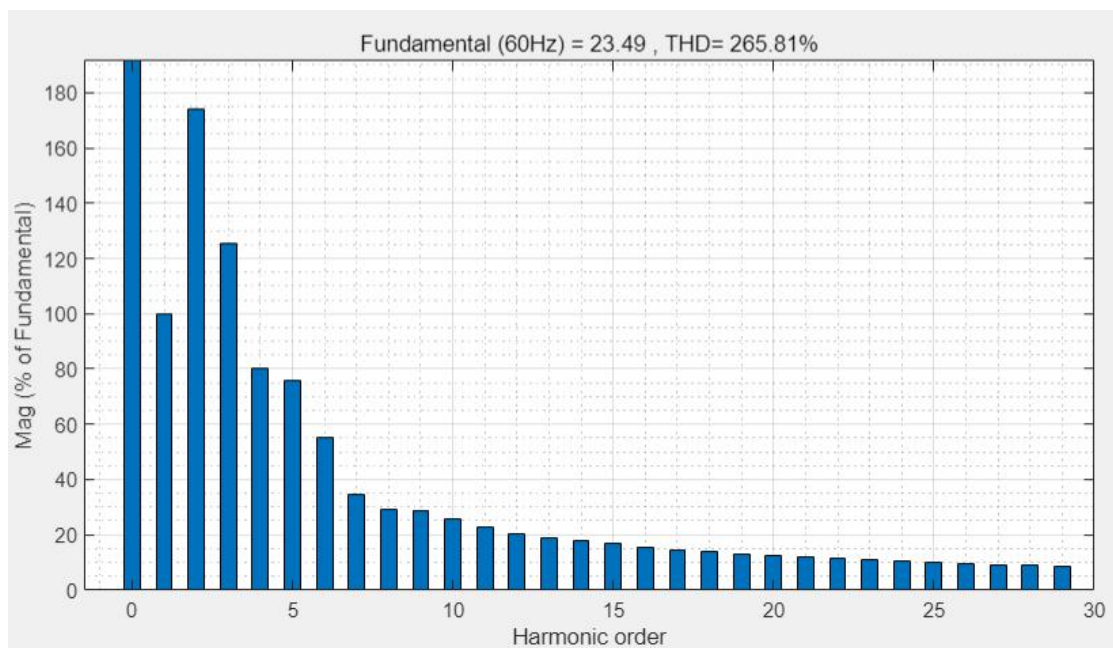


Fig. 14. The harmonic spectrum of Vd

3. Task 3

A Quarter Load - 500 ohms

$$G_v(s) \approx (4.263 + 0.086s)/s$$

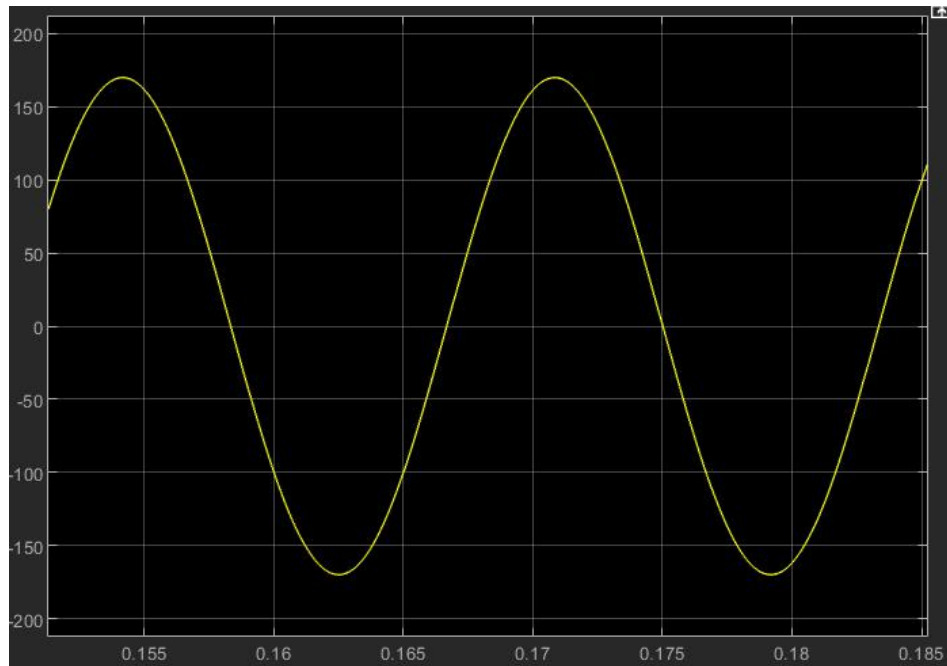


Fig. 15. Vs for A quarter load

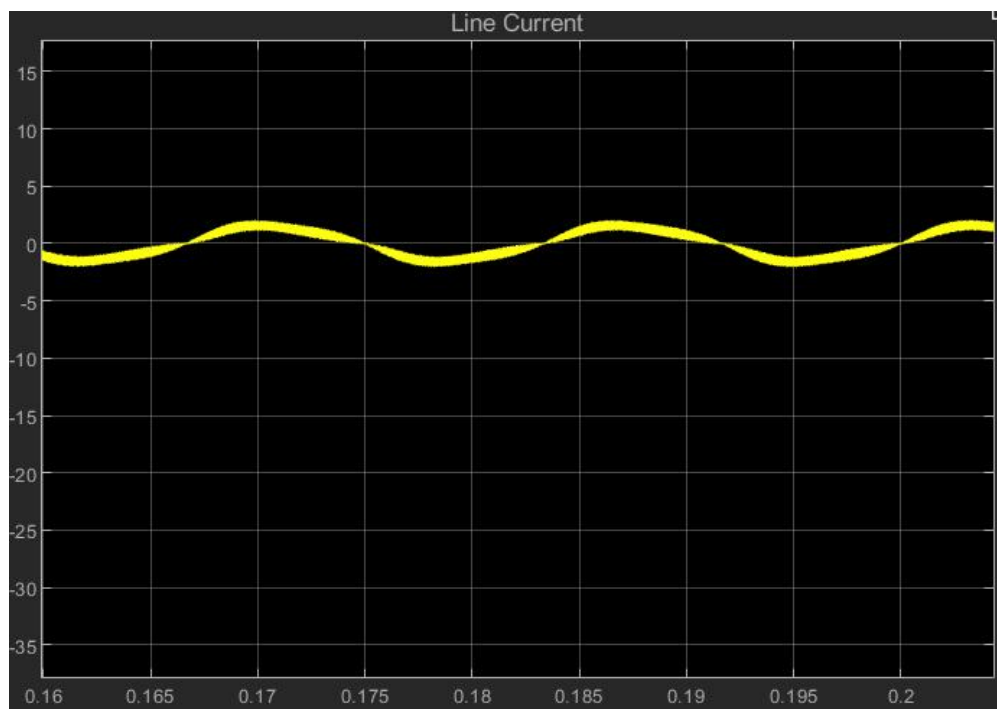


Fig. 16. Is for A quarter load
Power Factor=1

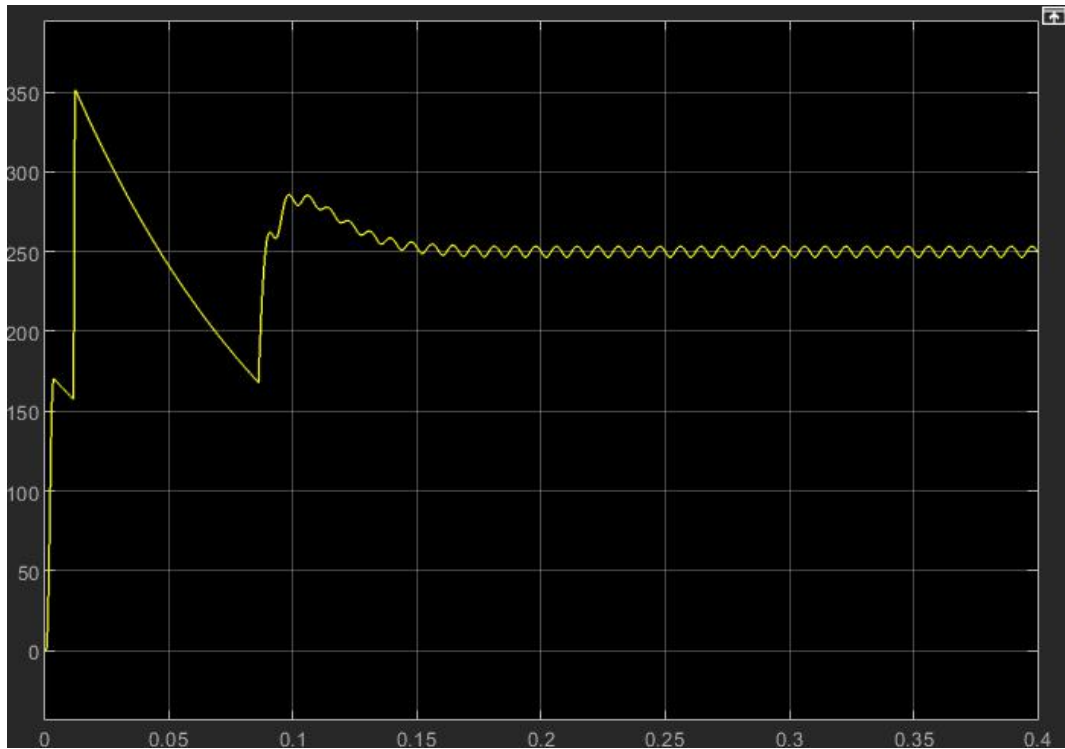


Fig. 17. V_d for A quarter load

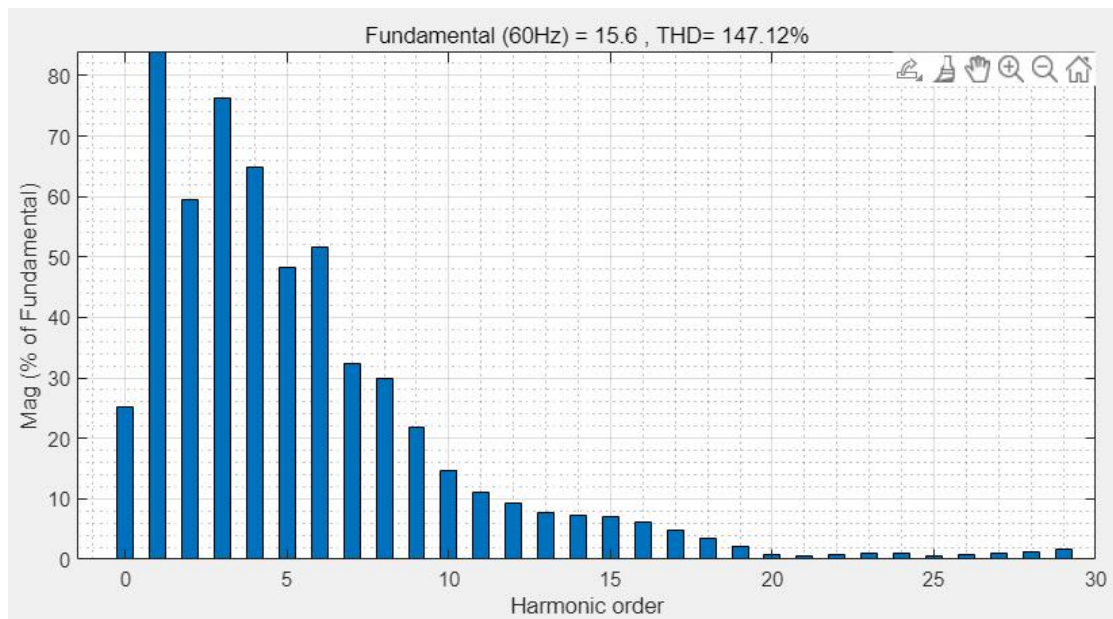


Fig. 18. The harmonic spectrum of I_s
THD of I_s = 147.12%

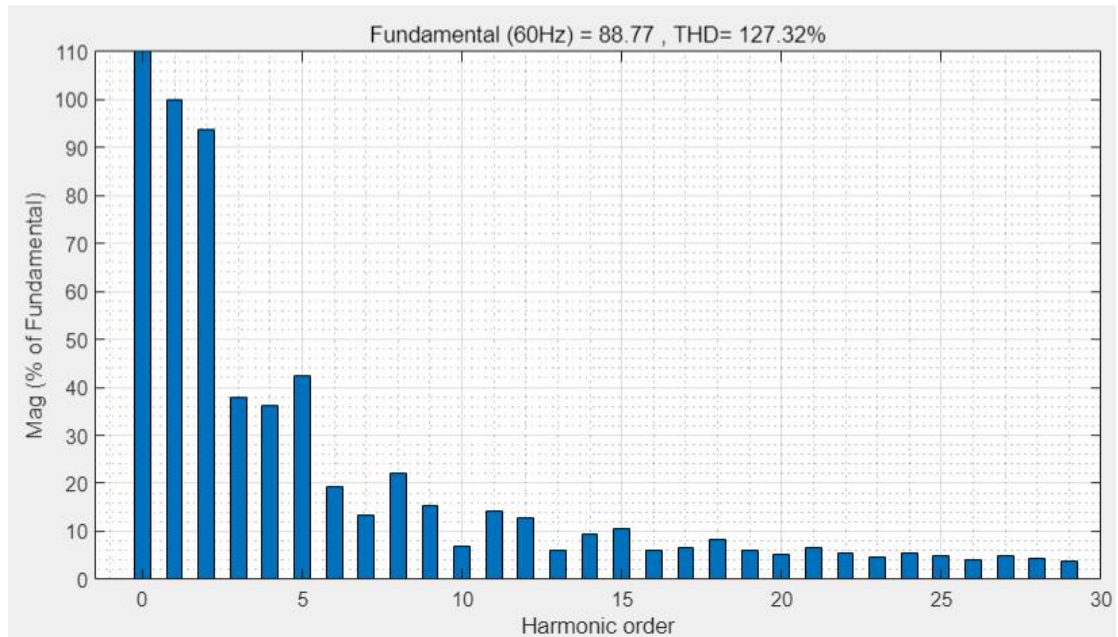


Fig. 19. The harmonic spectrum of Vd

2) Analysis

As we can see from the image, the output voltage rises quickly at the beginning, and the distortion signal appears for a short time. Through our control of the circuit, this value is quickly limited, and the output voltage and current both tend to the expected value. From our power Factor measurements, PF is always 1. With the increase of load resistance, THD of current is become greater.

Part C)

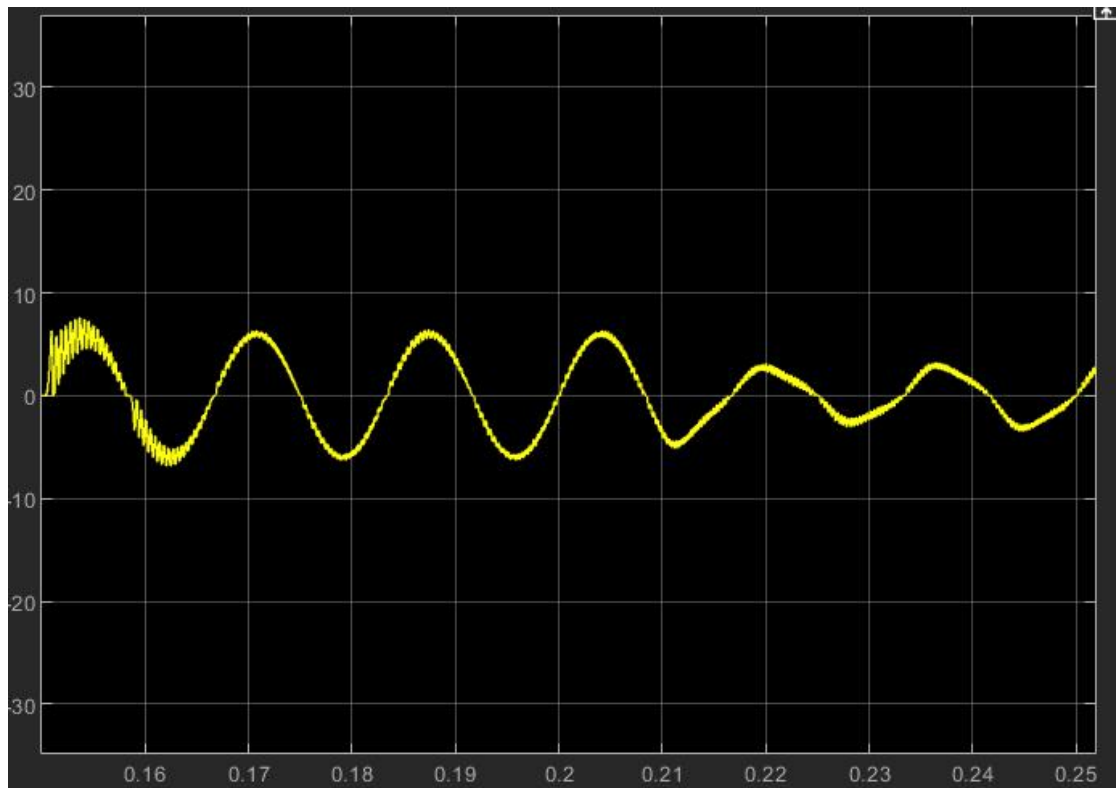


Fig. Is

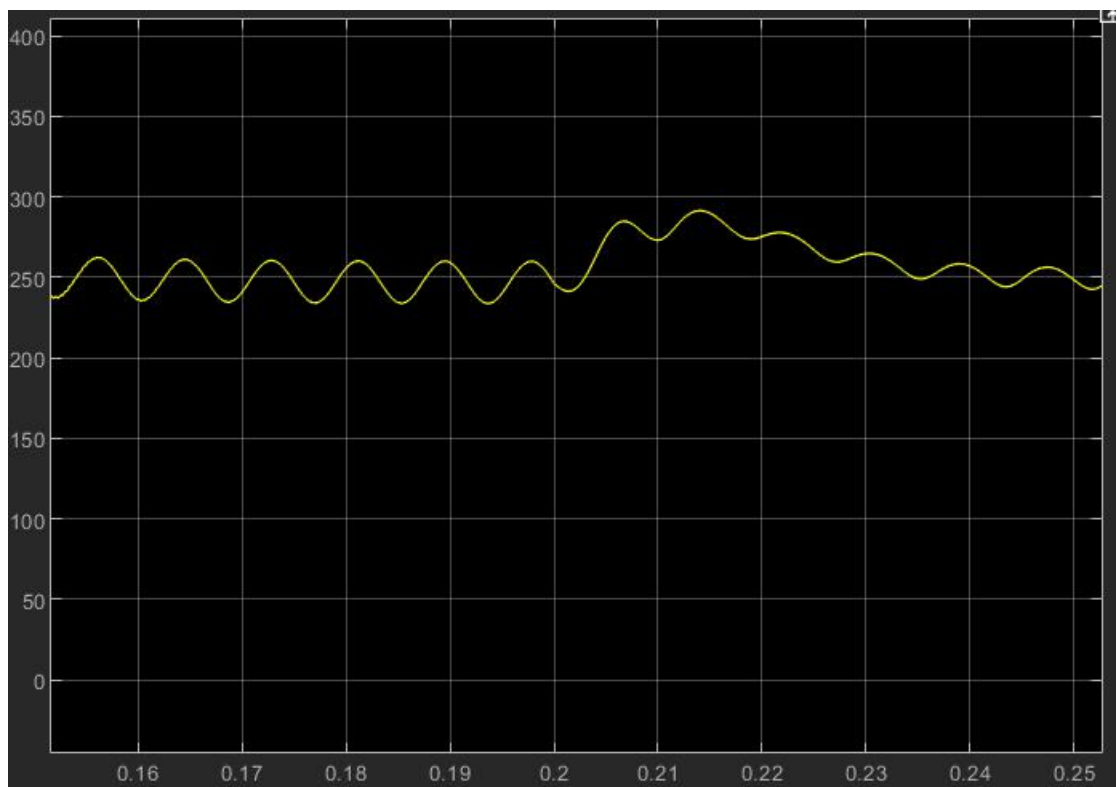


Fig. Vd

4. Conclusion

The purpose of the power factor correction circuit is to increase the conduction Angle of the rectifier so that the ac input current waveform is sinusoidal and in phase with the voltage waveform. In this project, I successfully use the feedback controller to control the circuit, and I can keep the steady of voltage an current. But there's only one downside that I can not use the max power to limit the circuit. Actually, I tried many different ways to limit the circuit, including the limit of inductance current and the limit of current output. I think maybe I still don't know how to use this knowledge. In the future, I will continue to focus on the resolution of this issue.